 


Name_____Date_____

Draw a *series circuit*. Label your picture with the following words:

battery wire light bulb

Circuit Diagram



How could you change your circuit to create a parallel circuit? Use complete sentences to explain the difference between a parallel and series circuit.

Draw a *parallel circuit*. Label your picture with the following words:

battery wire light bulb

Circuit Diagram



How could you change your circuit to create a series circuit? Use complete sentences to explain the difference between a parallel and series circuit.
